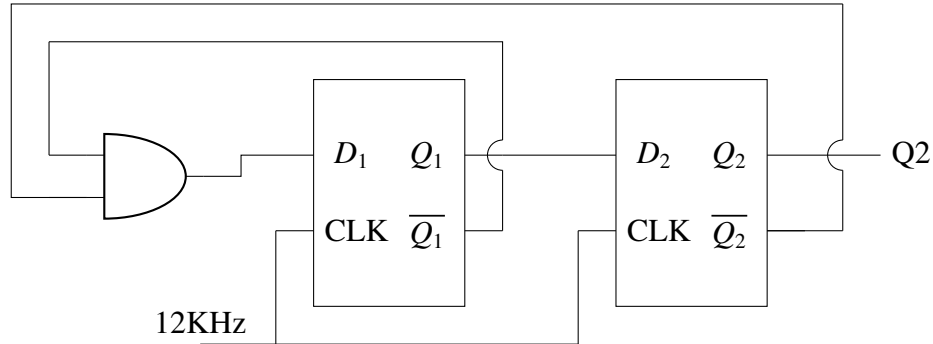



EC 25

EE23BTECH11048-Ponugumati Venkata Chanakya*

QUESTION: In the circuit shown, the clock frequency ,i.e.,the frequency of the clock signal,in 12 kHz. The frequency of the signal at Q_2 is ____kHz



Solution:

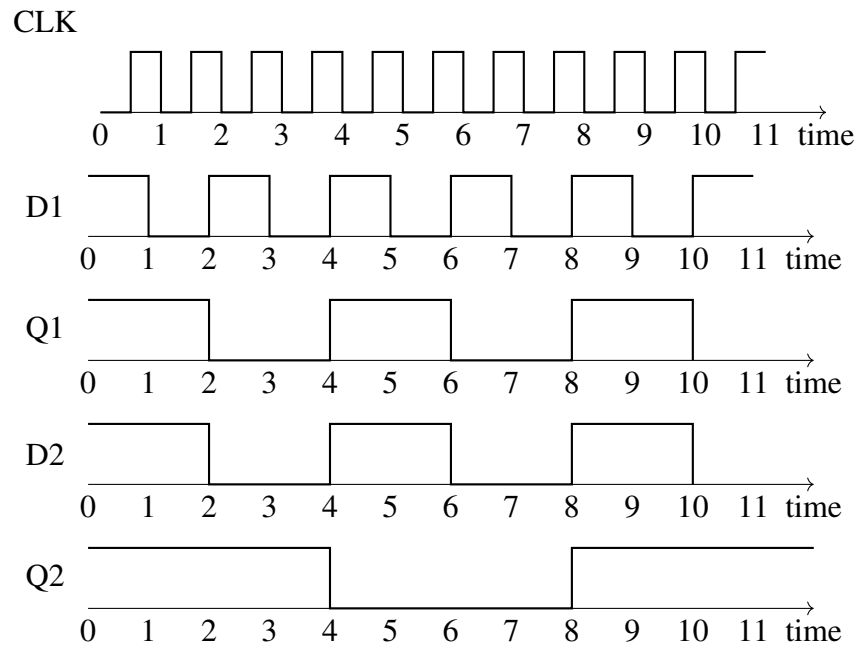

⇒ The frequency of the signal at Q_2 is 4KHz