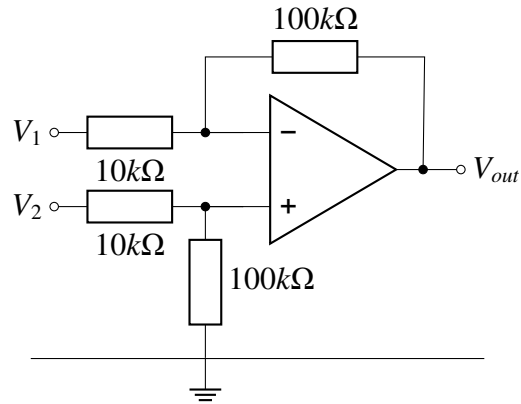


# EE 34

EE23BTECH11048-Ponugumati Venkata Chanakya\*

**QUESTION:** In the circuit below, operational amplifier is ideal. If  $V_1$  is 10mV and  $V_2$  is 50mV the output voltage ( $V_{out}$ ) is



- 1) 100mV
- 2) 400mV
- 3) 500mV
- 4) 600mV

GATE 2019 EE

**Solution:** Let  $V_3, V_4$  be values of voltages negative and positive terminal respectively  
For an ideal operational amplifier  $V_3 = V_4$

$$\begin{aligned}
 V_4 &= 0 + (V_2 - 0) \left( \frac{R_1}{R_1 + R_2} \right) \\
 V_4 &= \frac{R_1 V_2}{R_1 + R_2} \\
 V_3 &= V_{out} + (V_1 - V_{out}) \left( \frac{R_1}{R_1 + R_2} \right) \\
 V_3 &= \frac{10V_1 - V_{out}}{11} \\
 \Rightarrow \frac{R_1 V_1 - V_{out} R_2}{R_1 + R_2} &= \frac{R_1 V_2}{R_1 + R_2} \\
 V_{out} &= (V_2 - V_1) \frac{R_1}{R_2} \\
 V_{out} &= (50 - 10) \frac{100}{10} \\
 &= 400mV
 \end{aligned}$$